

Lab2-Exercises5 斐波那契数列

高政 11912015

1、简述

1.1、 实验目的



通过本实验了解带数据路径的有限状态机 (FSMD) 的基本设计流程, 学习 VHDL 语言中的 case 语句的使用。

1.2、 斐波那契数列

$$\text{fib}(n) = \begin{cases} 0 & \text{if } n = 0 \\ 1 & \text{if } n = 1 \\ \text{fib}(n-1) + \text{fib}(n-2) & \text{if } n > 1 \end{cases}$$

斐波那契数列的求解公式如上所示, 本次实验中输入 n 是一个六比特的二进制信号, 输出则是 43 比特的信号。

2、实验准备

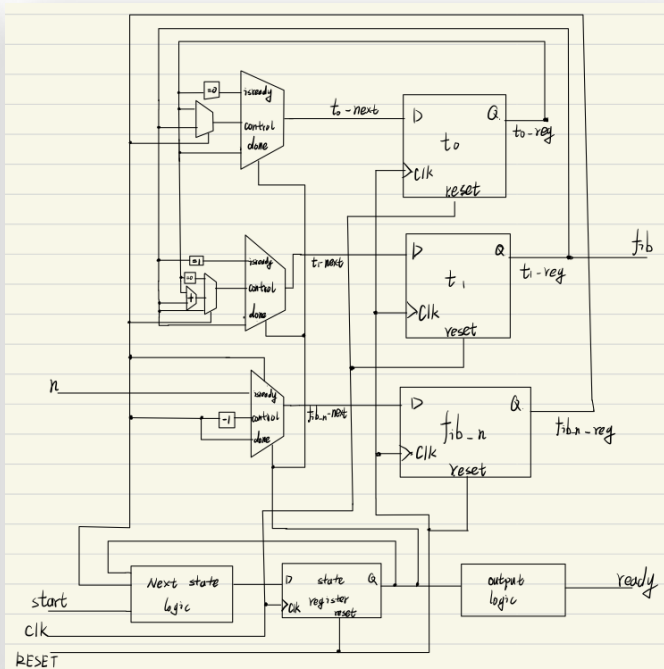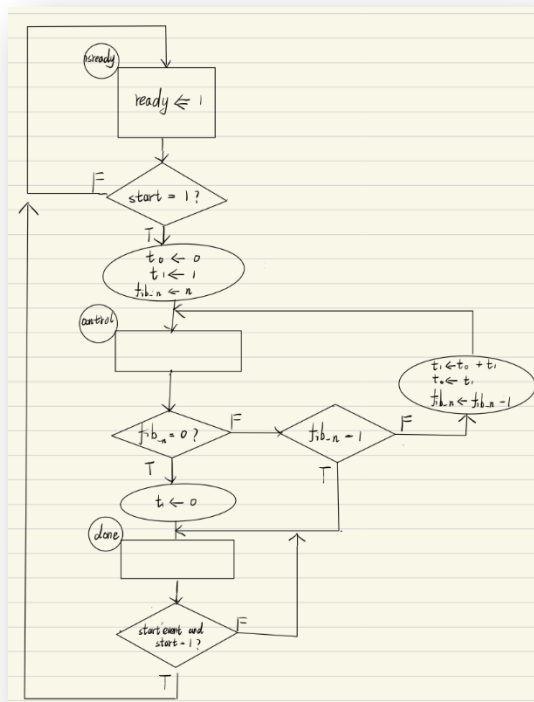

斐波那契数列的 ASM 框图如左上图, 其相应电路如右上图。

伪代码如下:

```
Fib(n):{  
    if (n = 0) then  
        fib = 0;
```

```

        else if (n = 1) then
            fib = 1;
        else {
            fib = Fib(n - 1) + Fib(n - 2);
        }
    }
}

```

3、VHDL 代码与 test bench 代码

斐波那契数列 VHDL 代码实现:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.std_logic_unsigned.all;
use IEEE.std_logic_arith.all;

entity fsmd is
    Port ( CLK : in STD_LOGIC;
          RESET : in STD_LOGIC;
          start : in std_logic;
          n : in STD_LOGIC_VECTOR (5 downto 0);
          ready : out std_logic;
          fib : out STD_LOGIC_VECTOR (42 downto 0));
end fsmd;

architecture Behavioral of fsmd is
    type state_type is(isready, contro, done);
    signal state, state_next : state_type;
    signal t0_next, t1_next, t0_reg, t1_reg : std_logic_vector(42 downto 0);
    signal fib_n_next, fib_n_reg : std_logic_vector(5 downto 0);
    signal do : std_logic;
begin
    clk_pro: process(CLK, RESET)is
    begin
        if RESET = '1' then
            state <= isready;
            t0_reg <= (others => '0');
            t1_reg <= (others => '0');
            fib_n_reg <= n;
        elsif (CLK'event and clk = '1')then
            state <= state_next;
            t0_reg <= t0_next;
            t1_reg <= t1_next;
            fib_n_reg <= fib_n_next;
        end if;
    end process clk_pro;

```

```

-- combinational circuit
process(state, state_next, t0_reg, t0_next, t1_reg, t1_next, fib_n_reg, fib_n_next) is
begin
    state_next <= state;
    t0_next <= t0_reg;
    t1_next <= t1_reg;
    fib_n_next <= fib_n_reg;
    ready <= '0';
    case state is
    when isready =>
        if start = '1' then
            t0_next <= (others => '0');
            t1_next <= (0 => '1', others => '0');
            state_next <= contro;
        else
            state_next <= isready;
        end if;
        ready <= '1';
    when contro =>
        if fib_n_reg = 0 then
            t1_next <= (others => '0');
            state_next <= done;
        elsif fib_n_reg = 1 then
            state_next <= done;
        else
            t0_next <= t1_reg;
            t1_next <= t0_reg + t1_reg;
            fib_n_next <= fib_n_reg - 1;
            state_next <= contro;
        end if;
    when done =>
        state_next <= isready;
    end case;
end process;
fib <= t1_reg;
end Behavioral;

    斐波那契数列 testbench 代码如下:
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity tb_fsmd is
end tb_fsmd;

architecture Behavioral of tb_fsmd is

```

```

component fsmd is
Port ( CLK : in STD_LOGIC;
      RESET : in STD_LOGIC;
      start : in std_logic;
      n : in STD_LOGIC_VECTOR (5 downto 0);
      ready : out std_logic;
      fib : out STD_LOGIC_VECTOR (42 downto 0));
end component;

--input
signal CLK : std_logic := '0';
signal RESET : std_logic := '0';
signal start : std_logic := '0';
signal n : std_logic_vector(5 downto 0) := "000000";

--output
signal ready : std_logic := '0';
signal fib : std_logic_vector(42 downto 0) := (others => '0');

constant per : time := 1 us;

begin
uut: fsmd
port map(
CLK => CLK,
RESET => RESET,
start => start,
n => n,
ready => ready,
fib => fib
);

clk_pro: process
begin
    CLK <= '0';
    wait for per/2;
    CLK <= '1';
    wait for per/2;
end process;

reset_pro: process
begin
    RESET <= '1';
    for i in 1 to 2 loop

```

```

wait until CLK = '1';
end loop;
RESET <= '0';
wait;
end process;

```


```

in_pro: process
begin
    start <= '1';
    n <= "111111";
    wait for 10*per;
    start <= '0';
    wait;
end process;
end Behavioral;


```

4、实验结果与分析


a) 行为仿真

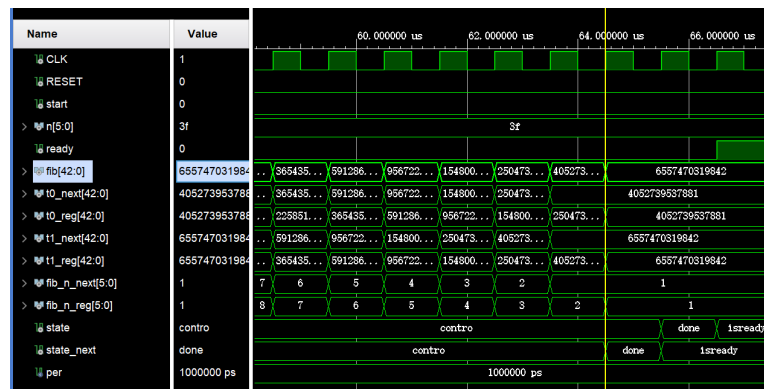


b) 综合后功能仿真

 


c) 综合后时序仿真

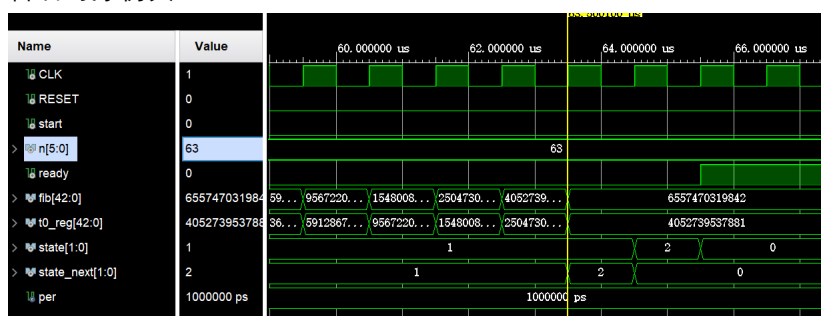

- d) 布线后功能仿真
- e) 布线后时序仿真

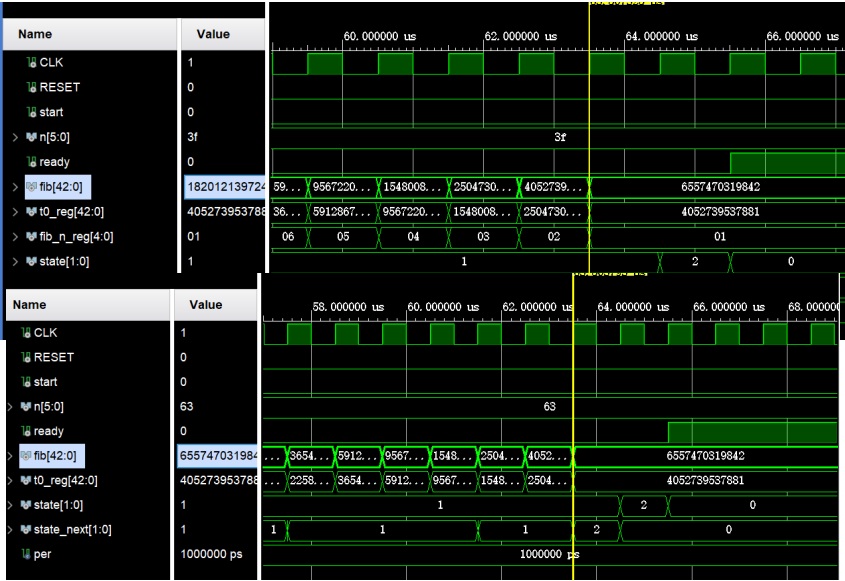


- f) RTL 原理图

 

由以上结果可以看出，代码基本实现预期目标，能够完成计算斐波那契数列的效果。

- g) 性能估计

 

经测试，本程序能正常工作的最短时钟周期为 63ns。

5、实验结论

通过本次实验我了解了 FSM 的基本设计流程和 VHDL 语句中的 case 语句的使用。